

MODULE 4: LEDs

SUMMER CHALLENGE

Electrical Engineering: Smart Lighting

Emre Ates

PhD Student

Boston University

ates@bu.edu




Overview

- From “Lighting” to Smart Lighting
- What is a Diode?
- LEDs!
- Electrical Power
- LED Drivers





Lighting & Color Science

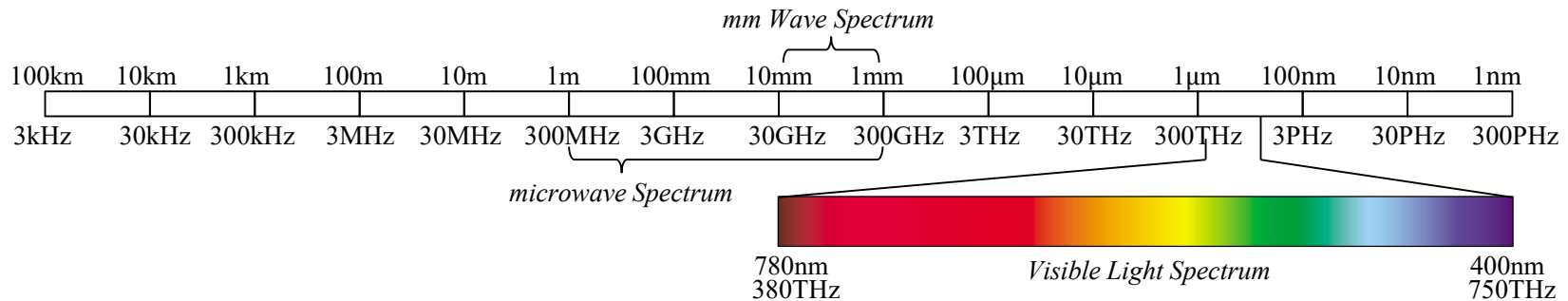- Visible Light is a form of electromagnetic radiation



- The human eye responds to the visible light spectrum
- White light is the presence of all colors


Human-Eye Response

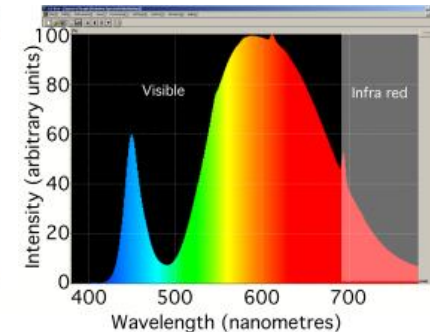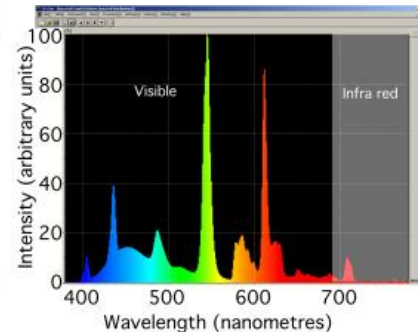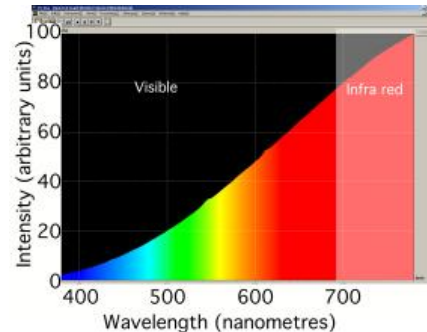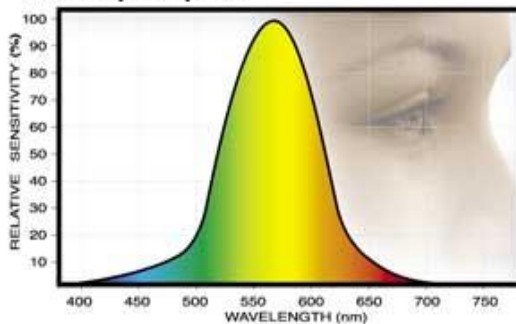



Smart Lighting

- In what ways can light be better?


- Energy Efficiency

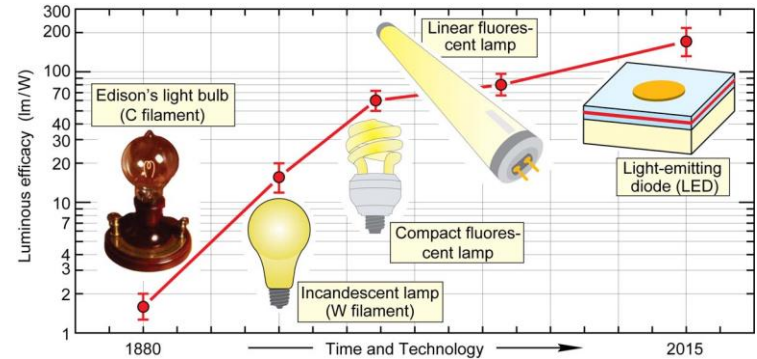

- Healthy Lighting

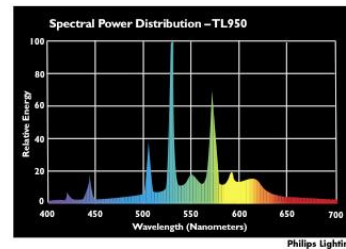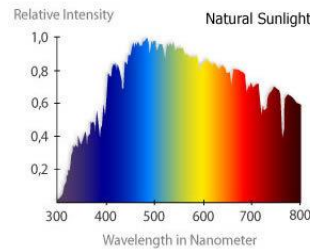

- Productivity (Data access)

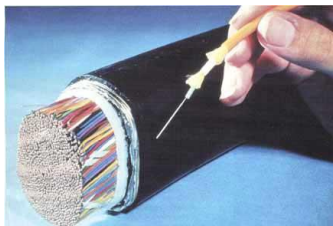



What is a diode?

- A device that allows current to flow in *one* direction



- Forward Bias Voltage

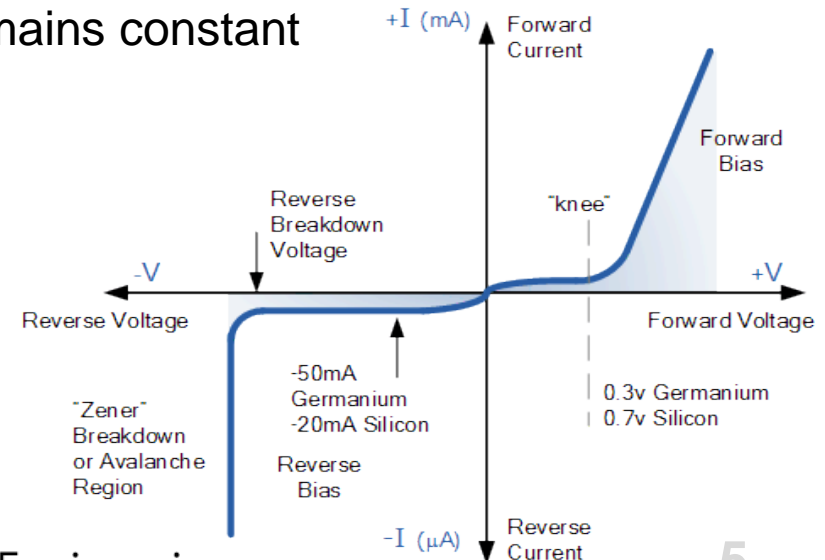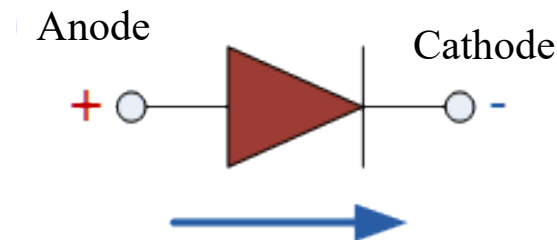
- For current to flow, diodes require a forward bias voltage
 - In an *ideal* diode, voltage drop remains constant



Kirchhoff's Voltage Law

- The algebraic sum of all voltages in a loop must equal 0


$$V_0 + (-V_1) + (-V_2) = 0$$

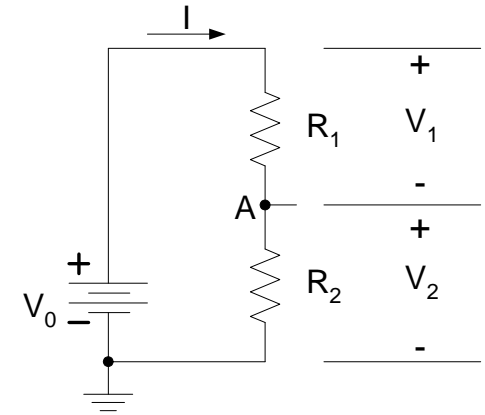

- Relationship to Diode circuits

- Once the diode reaches the turn on voltage, V_R increases with V_S
- Current through the circuit increases with V_R

$$V_S + (-V_D) + (-V_R) = 0$$

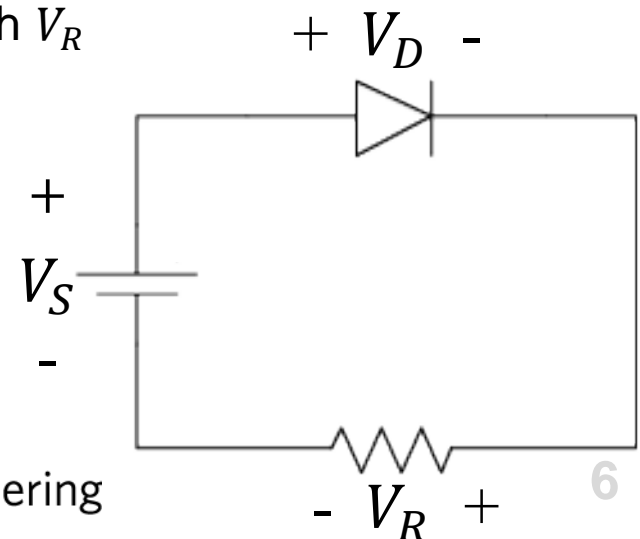

LEDs





David Miller

How Do LEDs Work?


- LED Materials
 - Semiconducting materials
 - Current can only flow in one direction
- Passing through the LED, electrons lose energy
 - Lost energy creates photons
 - Photons have discrete wavelength related to band-gap
- Band-gap width and energy
 - The wider the band-gap, the greater the energy of the photon released
 - Specialized materials & processes required to achieve wide band-gap
 - Planck's Relation:

$$E = \frac{hc}{\lambda}$$

Small Band Gap: Low Energy Red Light

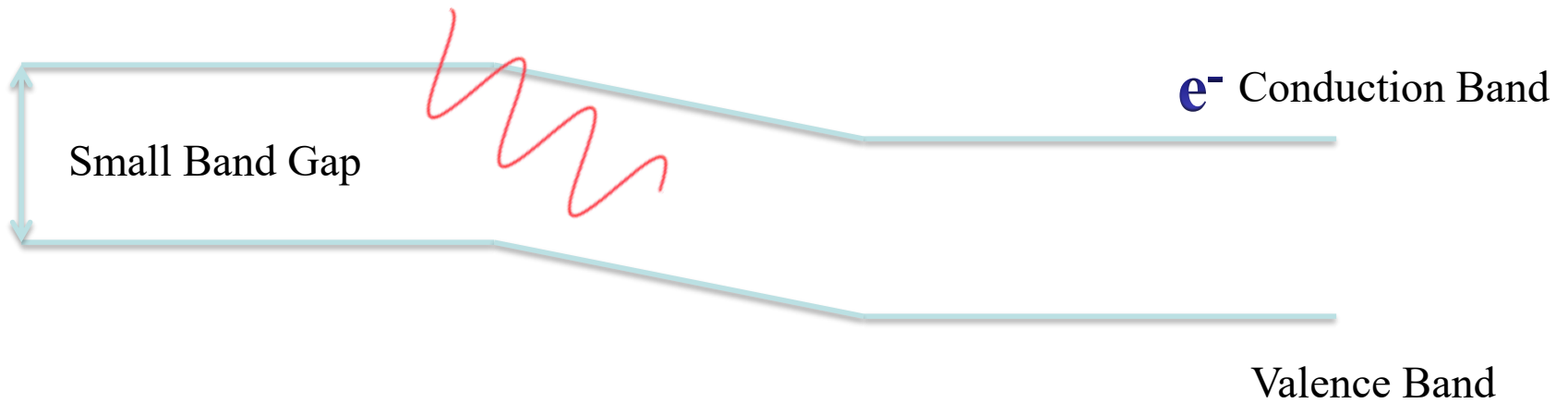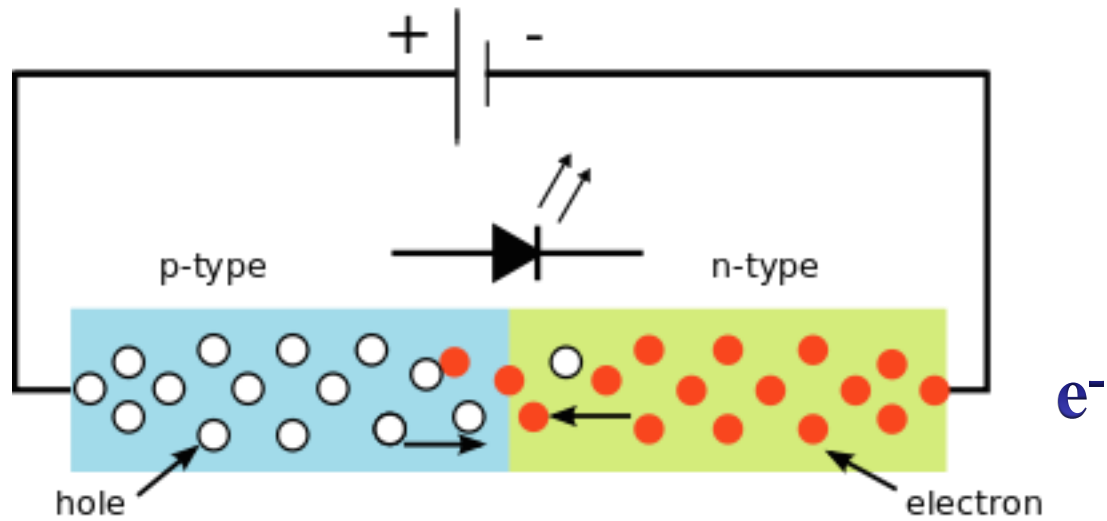

Large Band Gap: High Energy Blue Light

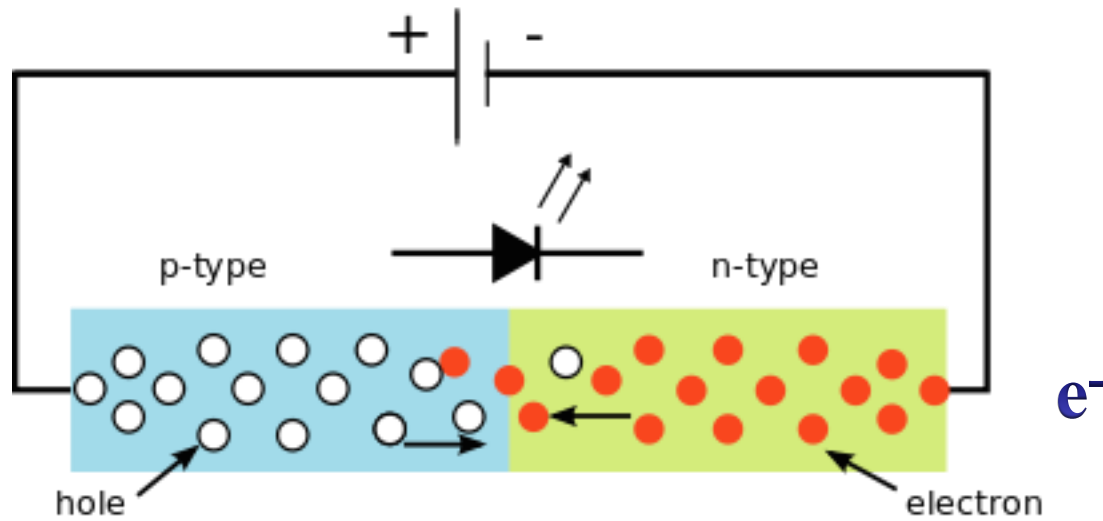

Experiment I


- LED circuit
- Determining the turn-on voltage

Electrical Power

- Power is the rate that energy is consumed.

$$P = VI \leftarrow \text{This is another one of those important equations...}$$

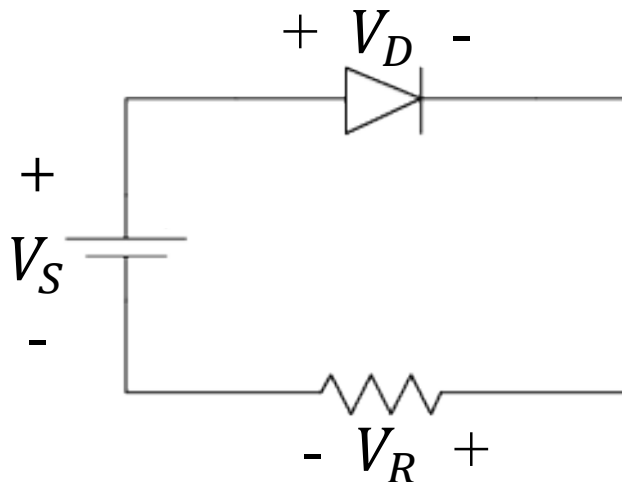- Power is measured in Watts [W] or [J/s]
- Energy *sources* (such as batteries) produce power while the *load* of the circuit absorbs power.



$$I = \frac{V_R}{R} = \frac{V_S - V_D}{R}$$

$$P_D = V_D I = \frac{V_D (V_S - V_D)}{R}$$


Electrical Power

$$V = IR$$

- Combining the previous equation with OHMS LAW:

$$P = VI = I^2R = V^2/R$$

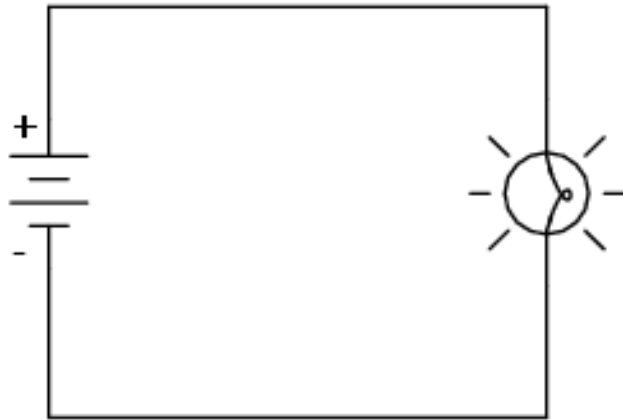- Consider a 60W incandescent attached to a 120V source
 - How does current change if you replace the 60W bulb with 120W bulb?



$$60 = 120^2/R_1 \qquad 120 = 120^2/R_2$$

$$R_2 = 120 = 0.5R_1$$

$$I_1 = \frac{V}{R_1} \qquad I_2 = \frac{V}{R_2} = \frac{V}{0.5R_1} = 2I_1$$

$$60 = 120I_1$$

$$120 = 120I_2$$

Experiment II

- LED Drivers
- Power Consumption

Recap

- What did you **LEARN** today?

