

MODULE 4: LEDs

BU SUMMER CHALLENGE Electrical Engineering: Smart Lighting Project


Beste Oztop
PhD Student
Boston University
boztop@bu.edu

Overview


- From “Lighting” to Smart Lighting
- What is a Diode?
- LEDs!
- Electrical Power
- LED Drivers

Lighting & Color Science

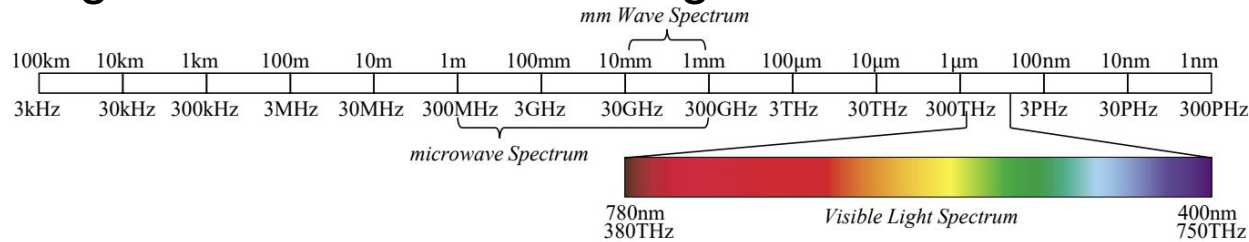- Visible Light is a form of electromagnetic radiation



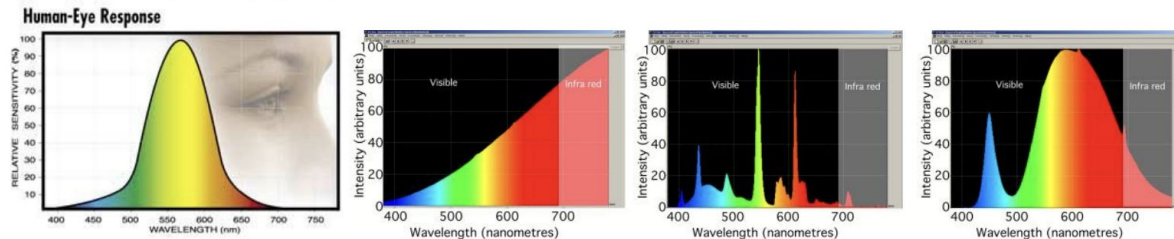- The human eye responds to the visible light spectrum
- White light is the presence of all colors



Smart Lighting

In what ways can using light be better?



- Energy Efficiency



- Healthy Lighting



- Productivity (Data access)

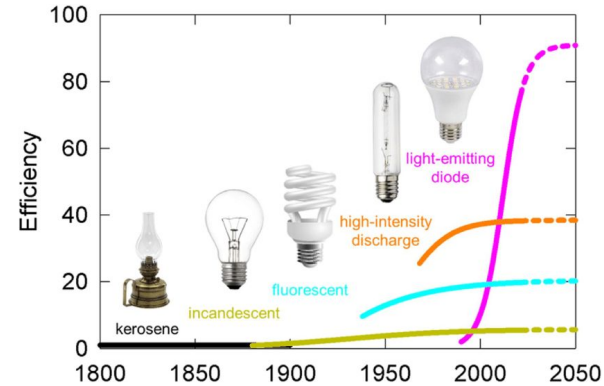
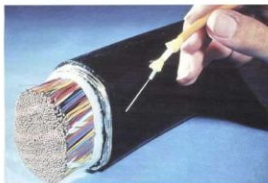


Boston University School of Engineering



What is a diode?

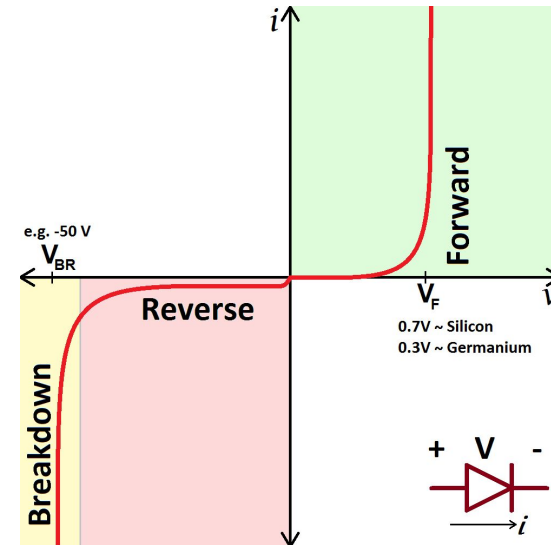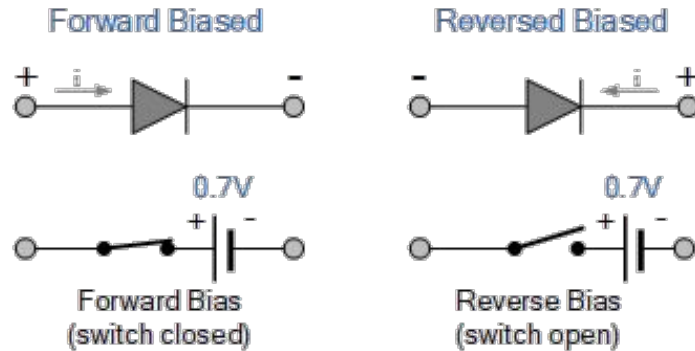- A device that allows current to flow in one direction and always has polarity (e.g., LED)
- Forward Bias Voltage
 - For current to flow, diodes require a turn-on voltage (i.e., forward bias voltage)
 - In an ideal diode, voltage drop remains constant





Kirchhoff's Voltage Law

The algebraic sum of all voltages in a loop must equal 0.


$$V_0 + (-V_1) + (-V_2) = 0$$

- Relationship to Diode circuits
 - Once the diode reaches the turn on voltage, V_R increases with V_S
 - Current through the circuit increases with increase in V_R

$$V_S + (-V_D) + (-V_R) = 0$$

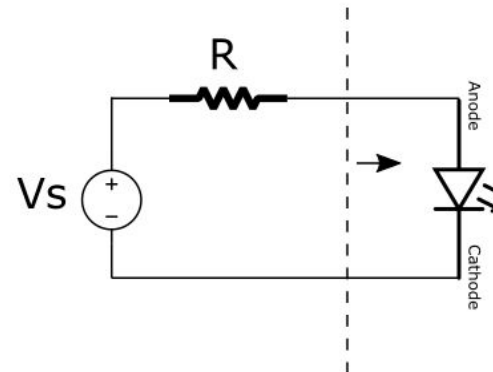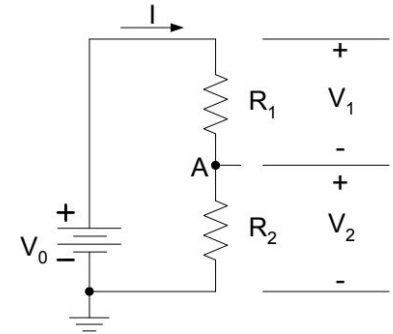

RC Circuits - The mystery of 'e'


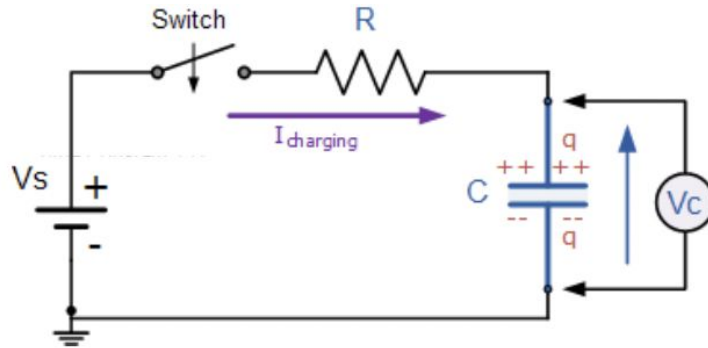


1. Kirchhoff's Voltage Law (KVL)
2. Ohm's Law
3. Capacitor Voltage
4. Current = Rate of change of charge
5. Substitute into KVL
6. Express $i(t)$ in terms of $Q(t)$
7. Rearrange to form a differential equation
8. Solve the differential equation


$$\tau \equiv RC$$
$$V_c = V_s(1 - e^{-t/\tau})$$

RC Circuits - Recap

Charge

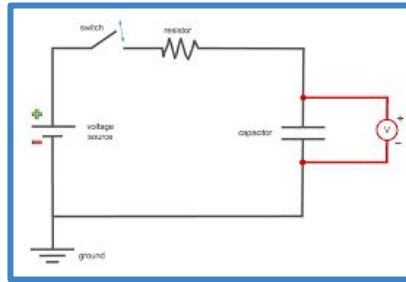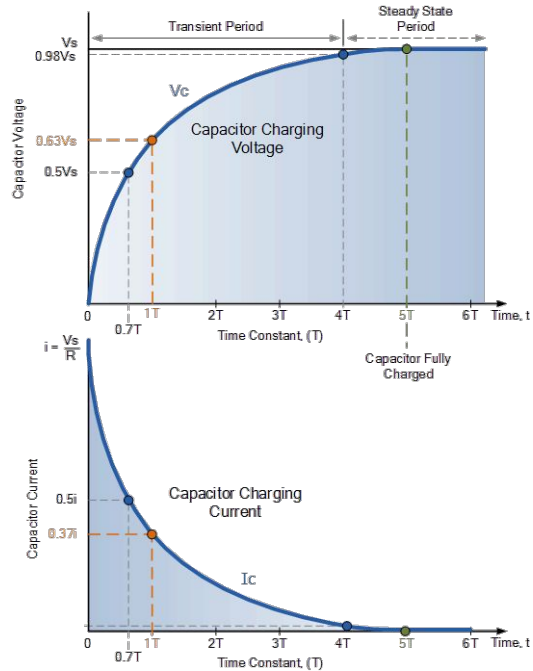

Discharge

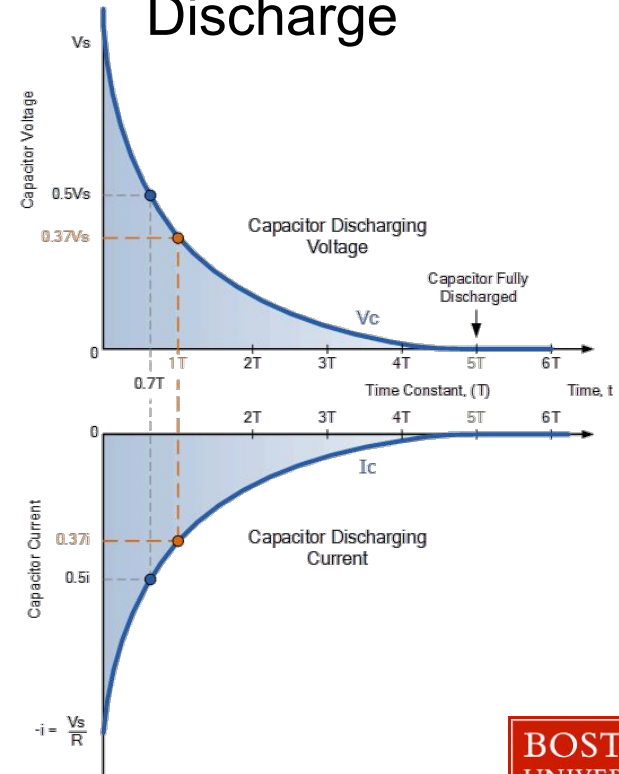


★ Reflect on what you learned so far!

- References:

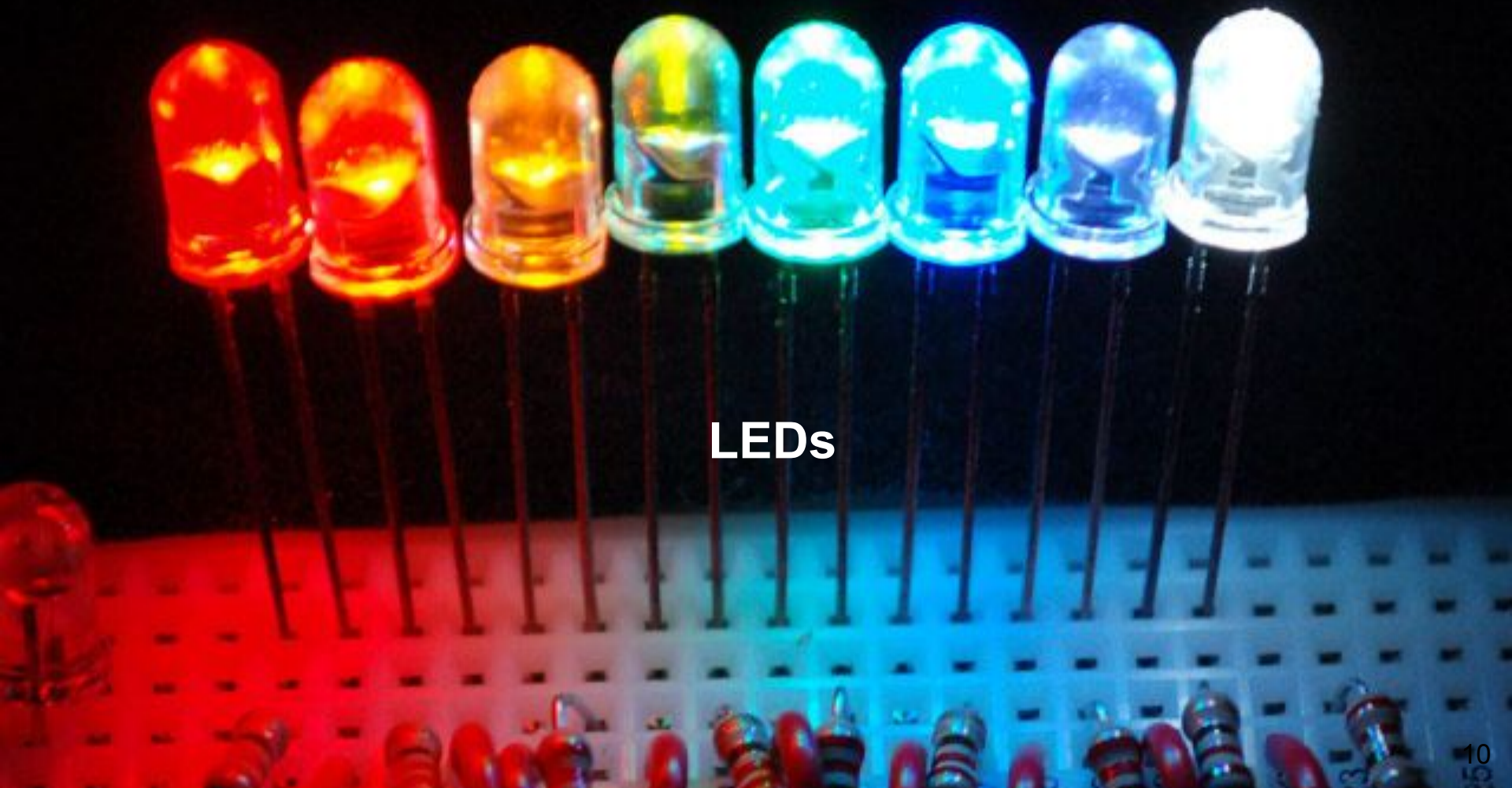- <http://www.physicsclassroom.com/>
- <http://www.allaboutcircuits.com/>





LEDs

How Do LEDs Work?


- LED Materials
 - Semiconducting materials: Resistance levels between those of a conductor and an insulator
 - Current can only flow in one direction
- Passing through the LED, electrons lose energy
 - Lost energy creates photons
 - Photons have discrete wavelength related to band-gap
- Band-gap width and energy
 - The wider the band-gap, the greater the energy of the photon released
 - Specialized materials & processes required to achieve wide band-gap

Planck's Relation


$$E = h\nu = \frac{hc}{\lambda}$$

where:

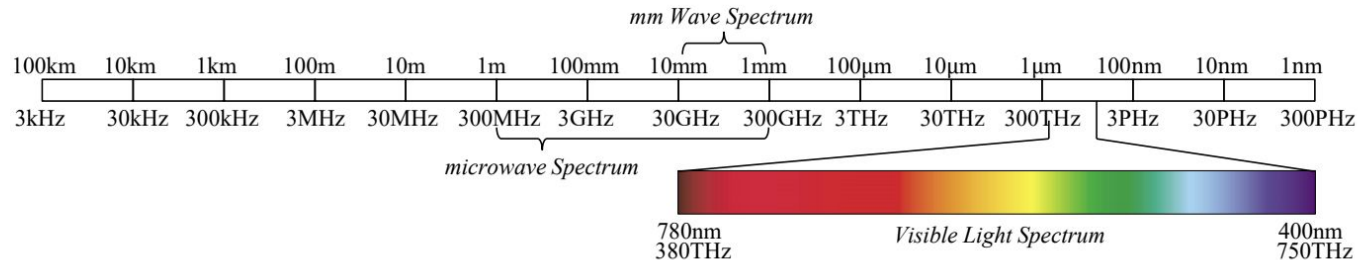
E = energy
h = Plank constant
ν = frequency
c = speed of light
λ = wavelength



Small Band Gap: Low Energy Red Light

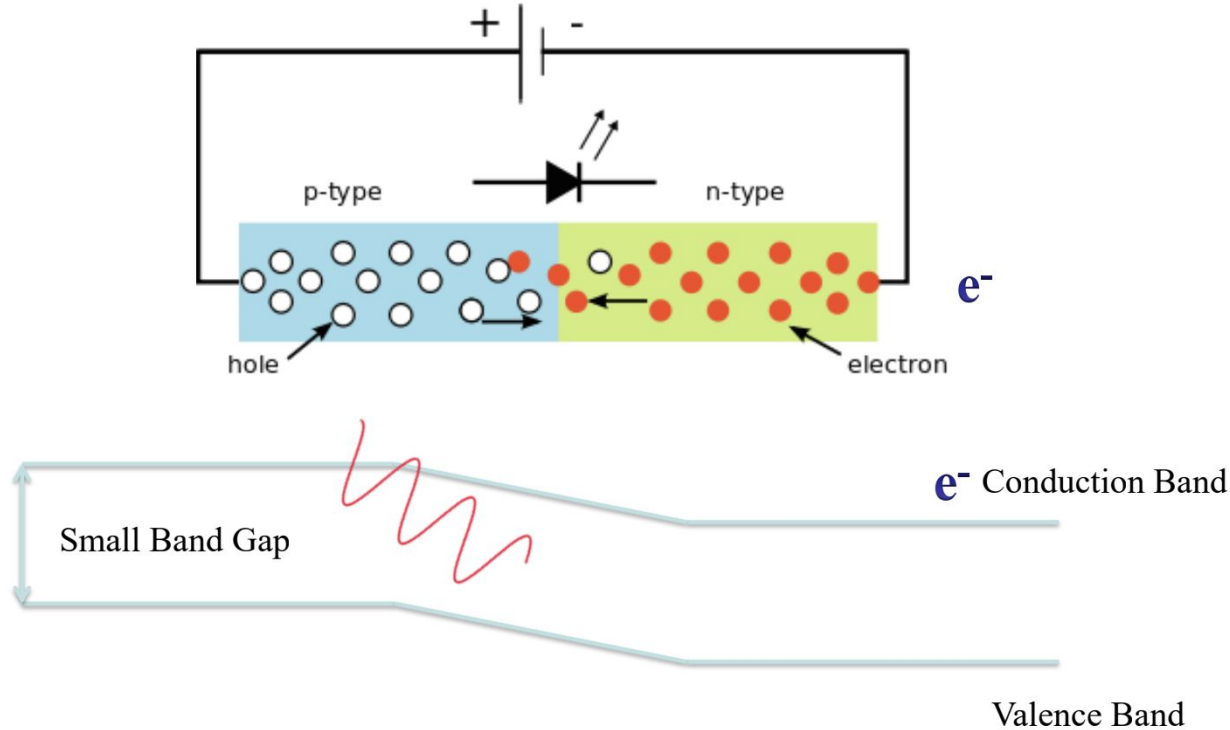

Large Band Gap: High Energy Blue Light

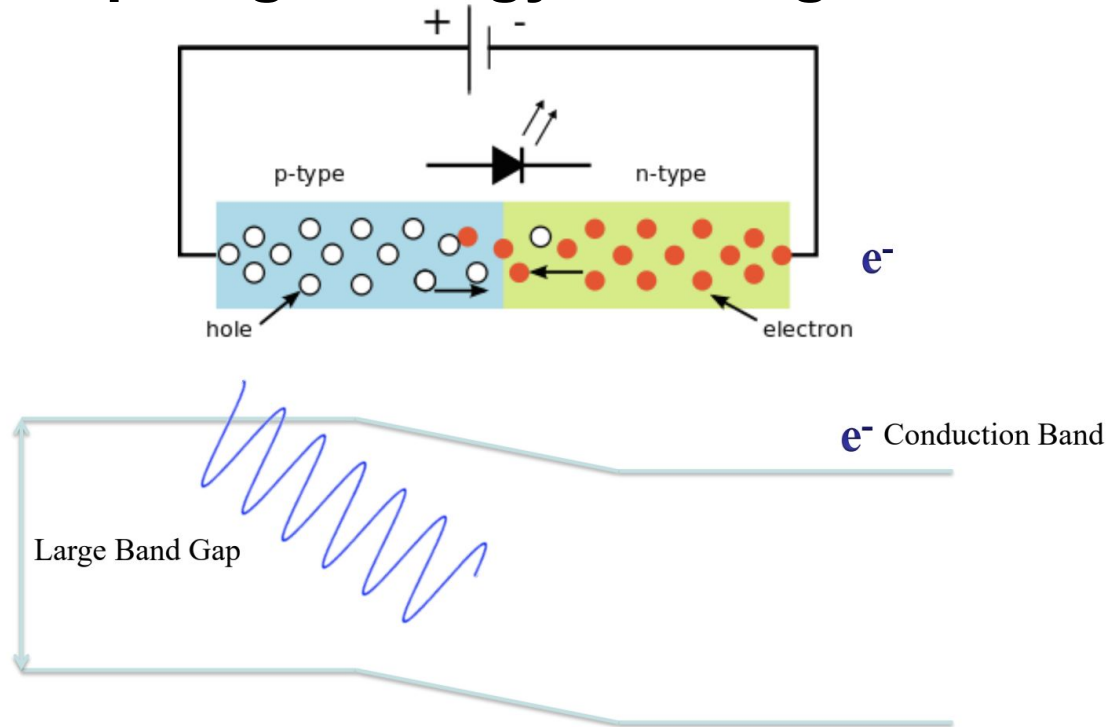

Experiment I


- Go to “**Lab Module 4: LEDs** “ in your experiment manual
- LED circuit
- Determining the turn-on voltage

Electrical Power

- Power is the rate at which energy is consumed.

$$P = VI$$

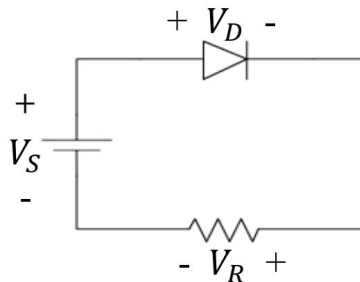- Power is measured in Watts [W] or [J/s]
- Energy sources (such as batteries) produce power while the load of the circuit absorbs power.



$$I = \frac{V_R}{R} = \frac{V_S - V_D}{R}$$

$$P_D = V_D I = \frac{V_D (V_S - V_D)}{R}$$

Electrical Power


$$P = VI$$

Combining the previous equation with Ohm's...

Law:

$$P = VI = I^2R = V^2/R$$

Exercise: Consider a 60W incandescent attached to a 120V source. How does current change if you replace the 60W bulb with 120W bulb?

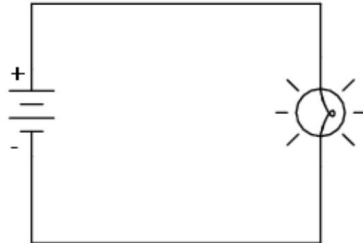

Experiment II

- LED Drivers
- Power Consumption

Reminder: Team Formation!

Think – Pair – Share

